 


Assignment 1

Due June 5, 13:59

Important: Late submissions will NOT be accepted. Please submit a hardcopy of your solutions in the ECE 466 **drop-box** (ELW, second floor) and your SystemC code via the ECE 466 **CourseSpaces** webpage, following the submission guidelines posted on the course website.

1. [10 points] Consider the SystemC code and the input waveforms of `clk`, `x1`, and `x2` shown below. Draw and briefly explain the corresponding output waveforms of `y1`, `y2`, and `y3`.



```
SC_MODULE (example) {

    sc_in <sc_logic> x1, x2;
    sc_out <sc_logic> y1, y2, y3;
    sc_in_clk clock;

    sc_signal <sc_logic> s;                                // signal "s"

    void example_process1() {
        sc_logic v;                                        // variable "v"
        v = ~s.read();                                    // ~ means NOT
        y1.write(x1.read() ^ v);                          // ^ means XOR
    }

    void example_process2() {
        sc_logic u;                                        // variable "u"
        u = ~x2.read();                                    // ~ means NOT
        y2.write(s.read() & u);                            // & means AND
    }

    void example_process3() {
        while(1) {
            s.write(x1.read() ^ x2.read());                // ^ means XOR
            y3.write(~s.read());                            // ~ means NOT
            wait();
        }
    }
}
```

```

SC_CTOR (example) {

    SC_METHOD(example_process1); sensitive << x1 << s;
    SC_METHOD(example_process2); sensitive << x2 << s;
    SC_CTHREAD(example_process3, clock.pos());


    s.write(SC_LOGIC_0);           // s initially 0
    y1.initialize(SC_LOGIC_0);     // y1 initially 0
    y2.initialize(SC_LOGIC_0);     // y2 initially 0
    y3.initialize(SC_LOGIC_0);     // y3 initially 0

}

};

```

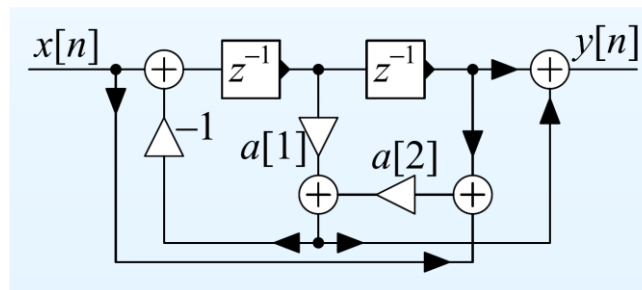2. [20 points] Consider the digital filter shown below, where z^{-1} means a delay of 1 clock cycle. In addition to the **clock** and **reset** inputs, the filter has one **float**-type input **x** and one **float**-type output **y**. Assume that the (multiplication) coefficients have the constant values $a_1 = 0.5$ and $a_2 = 0.25$, with $a_0 = -1$. First, create individual SystemC modules for the **float**-type adder, multiplier, and clocked z^{-1} register with reset. Then, create instances of these modules as needed and connect them together to obtain a top-level structural description of our filter. Next, introduce a clocked stimulus generator and a clocked result monitor: your testbench must start with a reset, then send a 1-cycle unit pulse to **x** and observe the pulse response on **y**. Finally, write `sc_main()` with waveform tracing of **reset**, **clock**, **x**, and **y** over 20 data samples. Your code submission must be self-contained, i.e., ready to be compiled/executed on the lab workstations. Submit an electronic copy of your solution via the ECE 466 **CourseSpaces** webpage (following the submission guidelines posted on the course website), and also submit a hardcopy in the ECE 466 **drop-box**.



3. [10 points] Given the same digital filter from the previous question, your task is to create its behavioral description using a single SC_MODULE with two processes: **SC_METHOD** (sensitive to **x** and the outputs of z^{-1} registers as needed, producing **y** and the inputs for z^{-1} registers as needed) and **SC_CTHREAD** (updating the outputs of z^{-1} registers at positive clock edges). This coding approach is similar to the way we describe Mealy-type FSMs (in our filter, **y** is directly affected by **x**). Submit both an electronic copy (**CourseSpaces**) and a hardcopy (**drop-box**) of your complete solution, with the same stimulus generator, result monitor, and `sc_main()` as in **Question 2**.