

Assignment 3


Due July 17, 13:59

Important: Late submissions will NOT be accepted. Please submit a hardcopy of your solutions in the ECE 466 **drop-box** (ELW, second floor) and your SystemC code via the ECE 466 **CourseSpaces** webpage, following the submission guidelines posted on the course website.

1. [10 points] Slides **6-10** of the “**Design**” lecture notes describe a UTF model using `sc_fifo` channels. Consider the **adder_out** channel connecting the **adder** output to the **fork** input. Your task is to perform the following communication refinement:

- (a) Replace `sc_fifo adder_out` with the hardware FIFO described on slides **36-37**.
- (b) Introduce the read adapter (see slide **39**) to interface the hardware FIFO with the **fork** input.
- (c) Merge the write adapter (see slide **38**) with the **adder** module, thus refining its output interface so that it connects directly to the hardware FIFO.
- (d) Put it all together (i.e., create new `sc_main`) and verify that your refined system model works correctly.

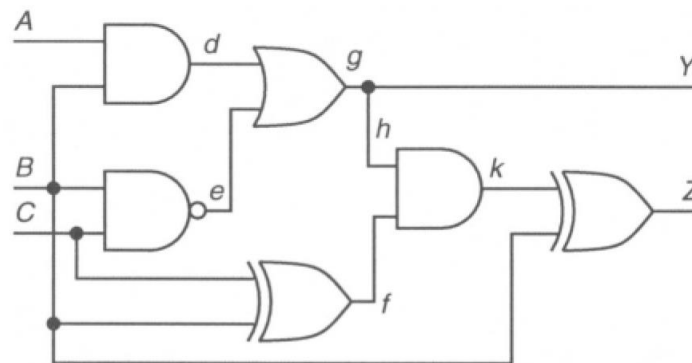2. [5 points] Using Boolean differences, obtain all 3-bit test vectors **ABC** detecting a stuck-at-0 fault on branch **h** in the logic circuit below.



3. [5 points] Consider an LFSR with the polynomial $f(x) = x^8 + x^5 + x^3 + x^2 + 1$. Show its standard and modular implementations.

4. [5 points] Slide **38** of the “**Test**” lecture notes shows a one-dimensional 5-cell CA circuit implementing the **90-150-90-150-90** rule structure. Show a CA circuit that implements the **150-150-90-90-150** rule structure instead (it produces all $2^5-1=31$ possible 5-bit nonzero patterns).

5. [5 points] Let the LFSR from **Question 3** be a response compactor accepting the following input from some circuit under test: **1011001111001101_{LSB}**.

(a) Show the signature computed by the LFSR.

(b) Show another input example producing the same signature as in (a).

6. [10 points] Let a multiple input signature register (MISR), with 4 inputs and characteristic polynomial $f(x) = x^4 + x^3 + 1$, accept the same 10-bit response sequence **0011001100_{LSB}** on all of its inputs.

(a) What is the signature computed by the MISR?

(b) Show the modular implementation of the MISR polynomial.

(c) Show another example of 4 inputs that yield the same signature as in (a).